



UNIVERSITY OF TEHRAN
Electrical and Computer Engineering Department
Digital Logic Design LAB
Lab1-Deliverables

1. Ring Oscillator

- Briefly explain the experiment procedure.
- Report the observed waveform along with the measured frequency of the chain.
- Report the propagation delay of the chain.
- Calculate the delay of a single inverter.

2. LM555 Timer

- Briefly explain the experiment procedure.
- For all three cases of R_2 resistor:
 - Include the waveform along with the measured frequency and duty cycle.
 - Using the equations provided in the manual, calculate the expected frequency and duty cycle to verify your measurement.
- Explain the changes in the duty cycle by varying the resistor R_2 .

3. Schmitt Trigger Oscillator

- Briefly explain the experiment procedure.
- Report the output frequency and calculate the α parameter for all three values of the resistor.
- Report the average α .

4. Synchronous Counter as a Frequency Divider

- Briefly explain the experiment procedure.
- Explain how can one determine the Parallel Input values of each counter.
- Explain the presetting mechanism used in the circuit.
- Report the observed waveform of the circuit output (MSB carry out) along with the measured frequency.
- Compare the output frequency with the Ring Osc. frequency and discuss the observed changes in the duty cycle.

5. T Flip-Flop

- Briefly explain the purpose of using TFF.
- Measure the output frequency and compare it with its input and the Ring Osc. frequency.